

 



## Input Synchronization

 


## start/stop Detect

 


## Registers

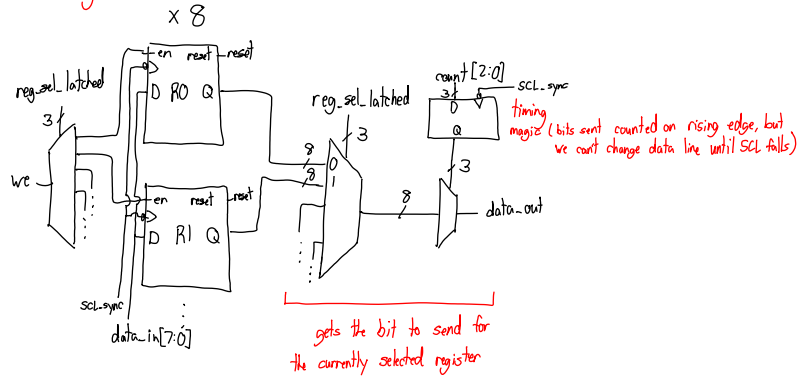

 
Latch the selected address so it can be accessed later




## Data Input

 

 (a handy counter for knowing when 8 bits have been sent/received)




## Output Generation

 


SDA pulled low if sending ack or if data\_out is low and the output is enabled

## Address Check

 


currently hardcoded but could come from a register

 ★ Note: All state transitions happen when a falling edge of SCL is detected, but both Reset and Init can transition on any edge



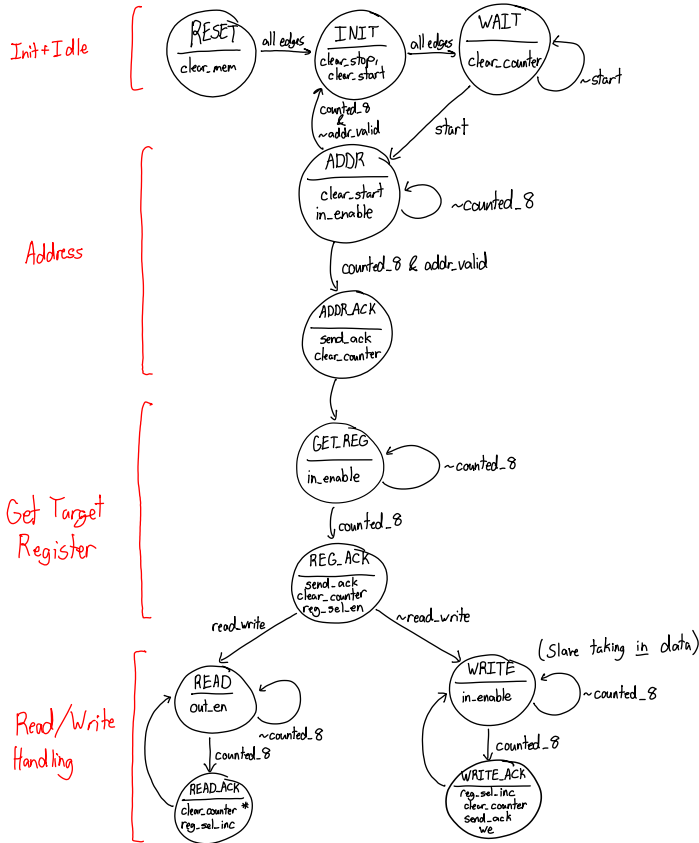★ All states besides RESET transition to INIT when stop is asserted



\* Need to double check but I believe the master sends the ACK. I don't think I need to do anything though, because immediately after a NACK will be a stop signal

