

 



## Input Synchronization

 


## start/stop Detect

 


## Registers

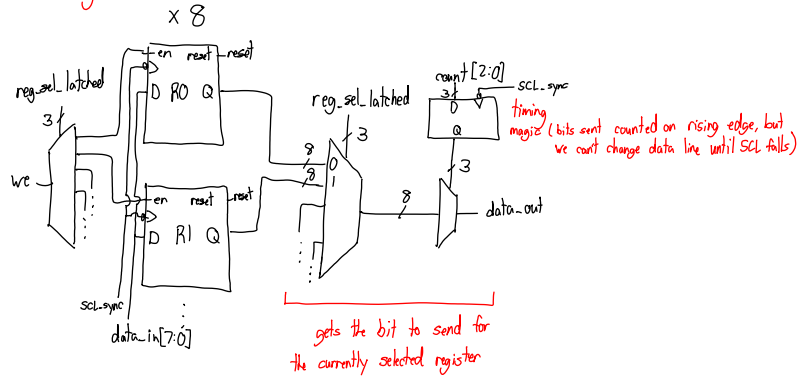

 
Latch the selected address so it can be accessed later




## Data Input

 

 
(a handy counter for knowing when 8 bits have been sent/received)



## Output Generation

 

## Address Check

 

currently hardcoded put could come from a register

$\rightarrow$  = all clock edges

→ = only clock edges when SCL is falling

\* All states besides RESET transition to INIT when stop is asserted  
All states transition to WAIT when start is asserted

